

A rectifier is an electronic circuit for converting ac voltage or current into a unidirectional de voltage or current. The voltage across the secondary forms the input voltage to the rectifier diode. This rectifier uses four diodes which conduct two half cycles of input as shown in figure 1. The AC voltage to be rectified is applied to the primary of the transformer. So this half cycle will be available at the output