

Open the switch across the power supply so that the capacitor starts to discharge through the. 1
multimeter. Draw a horizontal line to cut the curve at $0.37V_o$ and determine the value of the time constant
T. 9. Calculate the resistance of the multimeter on the 10V D.C. range. Record the final steady voltage
.(Vo).2.3.4.5.6.7.8