

A rectifier is an electronic circuit for converting ac voltage or current into a unidirectional dc voltage or current. The voltage across the secondary forms the input voltage to the rectifier diode. A half wave rectifier converts ac voltage into a pulsating dc voltage using only one half cycle of the applied ac voltage. The AC voltage to be rectified is applied to the primary of the transformer