

You can get different readings of the current I and voltage V by varying the battery source. Record the.2
value of the current through the resistance and the voltage across it. 5. Set the value of the voltage of the
.battery at a certain voltage. Repeat step 3 to get at least 10 different readings.3.4.6