

The prototype uses an NTC thermistor to sense heat. As heat rises, resistance drops, triggering the BJT and turning on the buzzer. Diagram blocks show each component's role