

In electrical circuits, components can be connected in two main ways: series and parallel. Parallel

Connection: In a parallel connection, components are connected across the same two points, so each component has the same voltage across it. The total current is divided among the parallel branches, and the total resistance in a parallel circuit is less than the smallest individual resistance. 1.2