

In order to improve the power factor, some device taking leading power should be connected in parallel with the load. This raises the power factor of the load. The power factor can be improved by connecting capacitors in parallel with the load operating at lagging power factor taking lagging current  $I$  at a power factor  $\cos \phi$