

In the circuit shown in Figure 3.7, MOSFETs QD3 and QD4 are used in synchronous rectification mode in order to reduce the forward voltage drop (V_F) of diodes D3 and D4 in the circuit of Figure 3.5.