

2. You can get different readings of the current I and voltage V by varying the battery source. Record the value of the current through the resistance and the voltage across it. 5. Set the value of the voltage of the battery at a certain voltage. Repeat step 3 to get at least 10 different readings. 3. 4. 6.