

Design and simulate a combinational circuit using the Quartus II simulator. Where X is the 4 bits– input