

Continuous current case In the continuous domain, the current in the diagram of an electric circuit is represented by an arrow. But the actual direction of movement of the electrons is the opposite of the positive direction of the current: Note: if after calculation in any branch, we find a negative sign of the value of I , this means that the real direction of the current is reversed compared to that chosen arbitrarily at the start.