

Goals of Experiment A. Studying the process of charging and discharging a capacitor. B. Calculating the time constant of a capacitors in two different methods (theoretically & graphically).