

Here's a suggested conclusion: Conclusion: The experiment confirms that the AND gate produces an output of 1 only when both inputs are 1. If either or both inputs are 0, the output is 0. This behavior aligns with the logical AND operation, as demonstrated in the truth table. Let me know if this works for you or if you'd like to adjust it!